

# **CIRCUIT DESIGN TO CONTROL THE BRIGHTNESS OF A LED – LED dimmer circuit**

## **CONTENTS:**

Introduction.....	3
Importance of circuit.....	3
Applications.....	3
Circuit Diagram.....	3
Block Circuit Diagram.....	3
Schematic Circuit Diagram.....	4
Materials Used.....	4
Actual Circuit.....	5
The Components: A Basic Overview.....	6
NE555 timer.....	6
Astable Mode.....	9
Understanding Duty Cycles.....	10
Duty Cycle.....	10
Duty Cycle calculation in our project.....	11
MOSFET.....	12
Potentiometer.....	13
LED.....	15
Working Explanation.....	17
Explanation.....	17
MOSFET purpose.....	18
PWM Control.....	19
No MOSFET.....	19
Demonstration of Project.....	21
What did we learn.....	25
Difficulties faced.....	25
Conclusion.....	26
References.....	26

## INTRODUCTION:

In our project, we have created a circuit to control the brightness of an LED using a potentiometer and a 555 timer IC. It is a handy way to adjust how bright or dim the LED shines. This report will give you a quick look at what we did, why we did it, where you can use it, and why it is important.

## Importance of the Circuit:

This circuit is important because it provides a simple and effective way to control the brightness of an LED. Being able to adjust the intensity of light is valuable in various situations, whether it is for creating a comfortable ambiance at home, conserving energy, or ensuring that LEDs meet specific lighting requirements.

## Applications:


You can use this circuit in many places, such as:

1. Home Lighting: To create the right mood or ambiance in your living space.
2. Energy Savings: Dimming the lights can help save energy, reducing electricity bills.
3. Automotive Lighting: In cars, you can adjust dashboard and interior lighting for better visibility and comfort.
4. Display Panels: For controlling the brightness of displays and indicators.
5. Stage and Event Lighting: To create dramatic lighting effects.
6. Street Lighting: To adjust the brightness of streetlights depending on the time of day.
7. Decorative Lighting: For art installations and decorative lighting.


This circuit's adaptability and simplicity make it a versatile solution for various lighting control needs.

## CIRCUIT DIAGRAM:

### Block Circuit Diagram:

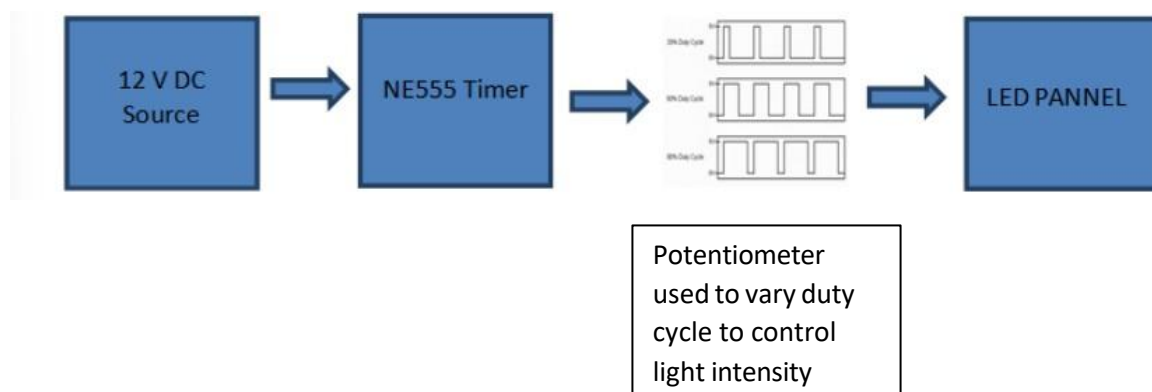

### Schematic Circuit Diagram:


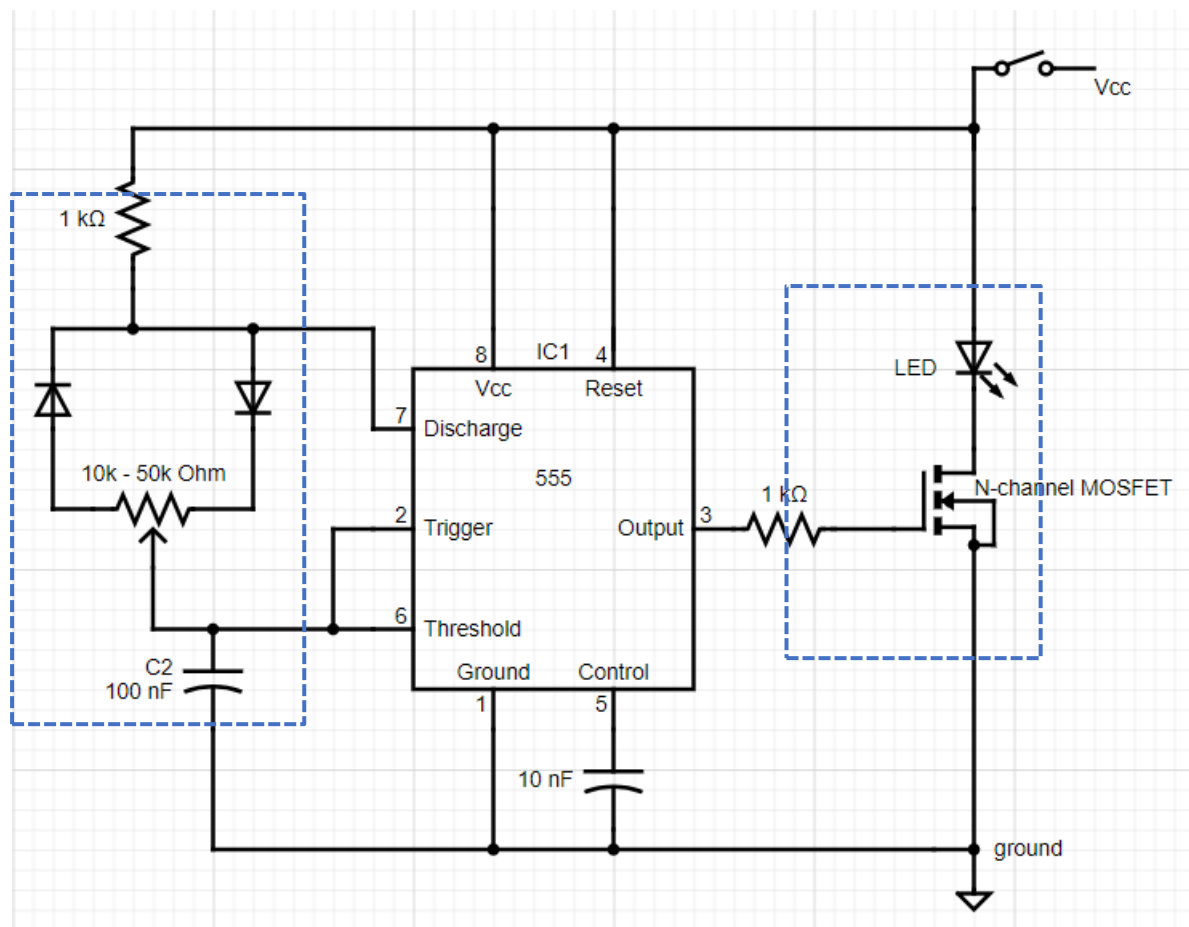


### MATERIALS USED:

Item	Specification	Quantity	Cost (Rs)
NE555 IC		1	10
Diodes		2	2 * 2 = 4
Capacitors	100nF	1	10
	10nF	1	5
Resistors	1kOhm	2	3 * 2 = 6
Potentiometer	10k – 50kOhm	1	40
MOSFET	N-Channel	1	50
LED	Green	1	2
Toggle Switch		1	5
Breadboard		1	100
Connecting wires			
Power supply DC	That can supply 5V	1	

Total estimate: Rs250


# ACTUAL CIRCUIT:

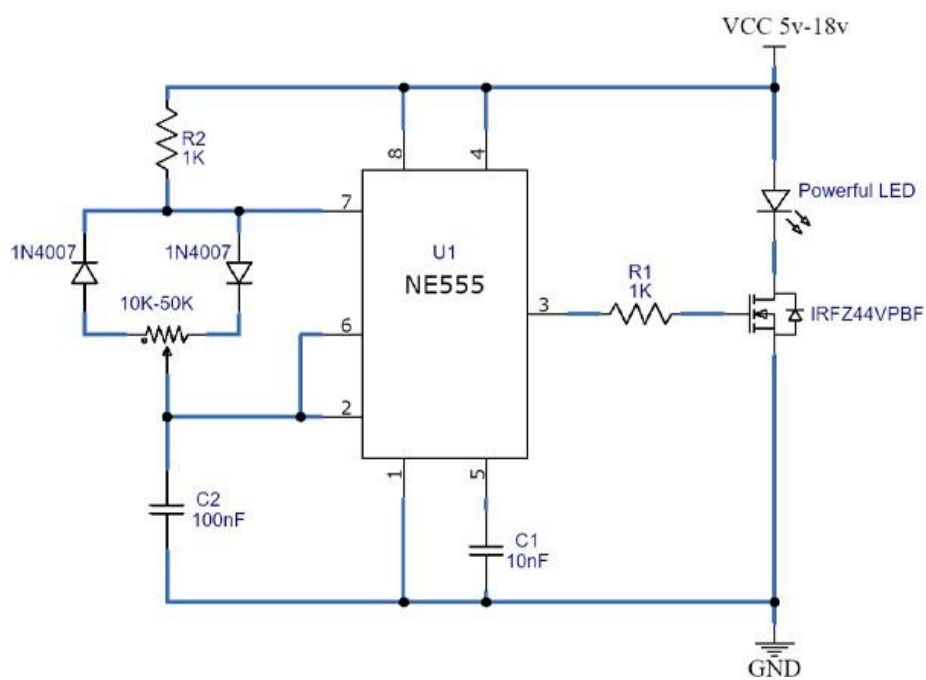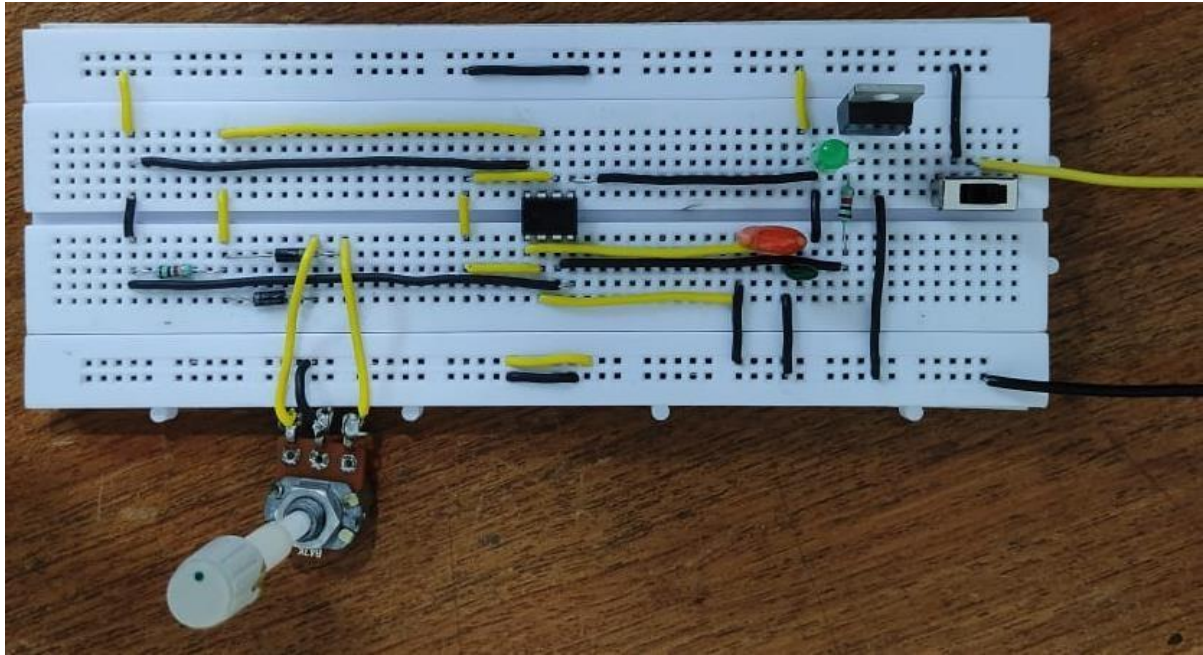

reference circuit from website

## THE COMPONENTS: A BASIC OVERVIEW:

### NE555 Timer:

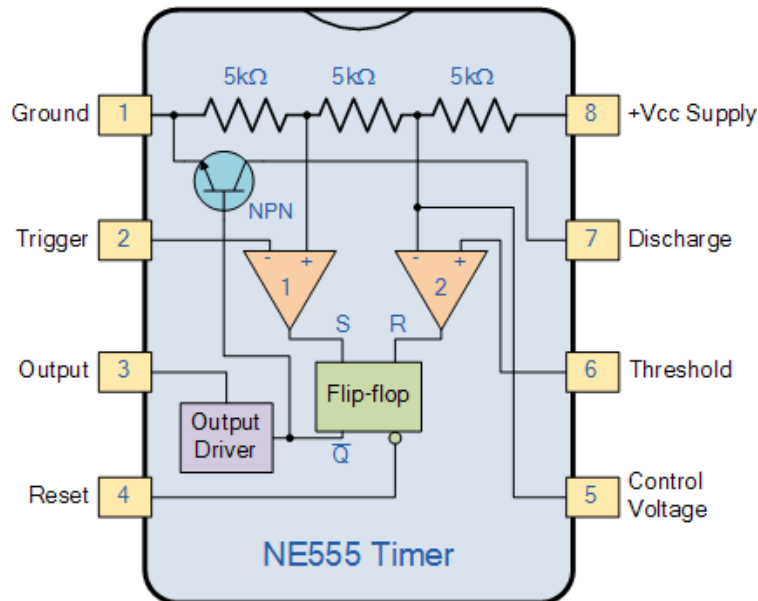

### Basic Understanding and Working of the NE555 IC for LED Brightness Control:

The NE555 integrated circuit (IC) is a versatile and widely used timer IC that plays a fundamental role in our project for LED brightness control. It operates as an astable multivibrator, providing precise timing and pulse generation, which is essential for regulating the LED's intensity. Here is a simplified theory of how the NE555 IC works within this project:

### 1. Timer Function:

The NE555 IC primarily acts as a timer. In our project, this timer function is harnessed to control the on and off periods of the LED, thereby altering its brightness.

## 2. Astable Mode:

The NE555 can be configured in an astable mode. In this mode, it continuously oscillates between two voltage levels, generating a square wave output. This square wave serves as the control signal to modulate the LED's brightness.

### 3. Key Components:

- R1 and R2 (Potentiometer): These resistors determine the timing of the square wave. By adjusting the potentiometer (R2), we can vary the resistance, which, in turn, changes the timing and controls the LED's brightness. This is achieved by regulating the charging and discharging times of a connected capacitor (C).
- Capacitor (C): The capacitor, in conjunction with R1 and R2, sets the frequency of the square wave. This frequency governs how fast the LED cycles on and off. A larger capacitor or different capacitor values can result in slower changes in brightness.

- Threshold (TH) and Trigger (TR) Inputs: The TH and TR inputs of the NE555 are critical. When the voltage at the TR pin is less than  $\frac{1}{3}$  of the supply voltage, the output flips to high, turning on the LED. As the voltage at the TH pin exceeds  $\frac{2}{3}$  of the supply voltage, the output goes low, turning off the LED. Adjusting R1 and R2 directly affects these threshold voltages, allowing us to control the LED's brightness.

#### 4. Pulse Width Modulation (PWM):

The continuous square wave output from the NE555 provides a Pulse Width Modulated (PWM) signal. PWM is a method for controlling the average power delivered to the LED. By altering the duty cycle (the ratio of the on-time to the total cycle time) of the square wave, we effectively adjust the LED's brightness. This dynamic control ensures smooth dimming of the LED.

#### 5. Significance in LED Brightness Control:

The NE555 IC is significant in our LED brightness control project because it offers a simple and effective means to regulate the LED's illumination. By altering the resistance and capacitance values in the circuit, we can precisely control the on/off periods of the LED. This, in turn, provides smooth and dynamic dimming, catering to various lighting requirements. The NE555's ability to generate a PWM signal is crucial in achieving this dynamic control, making it a key component in our project for LED brightness control.

#### Pinout of NE555:

555 Timer pin number	Pin name	Pin direction	Pin description
1	GND	Power	Ground Supply: This pin serves as the ground reference voltage (zero volts).
2	TRIGGER	Input	Trigger: When VTRIGGER falls below $\frac{1}{2}$ VCONTROL ( $\frac{1}{3}$ VCC, except when CONTROL is driven by an external signal), OUTPUT goes to the high state, and a timing interval starts. As long as TRIGGER continues to be kept at a low voltage, OUTPUT will remain in the high state.
3	OUTPUT	Output	Output: This pin functions as a push-pull (P.P.) output, transitioning to either a low state (GND) or a high state (VCC minus approximately 1.7 volts for bipolar timers). Bipolar timers can provide a current of up to 200 mA through this pin. In the case of bipolar timers, when this pin is connected to an edge-sensitive input of a digital logic chip, it may be necessary to add a decoupling capacitor with a capacitance of 100 to 1000 pF between this pin and GND to prevent double triggering.

4	RESET	Input	Reset: A timing interval can be reset by bringing this pin to a GND connection, but the timing does not recommence until this pin rises above approximately 0.7 volts. This pin takes precedence over TRIGGER, which, in turn, overrides THRESHOLD. If this pin is not utilized, it is advisable to connect it to VCC to prevent unintended electrical noise from triggering a reset.
5	CONTROL	Input	Control: This pin allows access to the internal voltage divider, which defaults to $\frac{2}{3}$ VCC. Applying a voltage to this pin enables the adjustment of timing characteristics. In astable mode, this pin can be employed to frequency-modulate the OUTPUT state. To prevent electrical noise from affecting the internal voltage divider, if this pin is not in use, it is recommended to connect it to a 10 nF decoupling capacitor between this pin and GND.
6	THRESHOLD	Input	Threshold: When the voltage at this pin exceeds VCONTROL (which defaults to $\frac{2}{3}$ VCC, except when CONTROL is influenced by an external signal), it concludes the high state timing interval, leading OUTPUT to transition to the low state.
7	DISCHARGE	Output	Discharge: This pin serves as an open-collector (O.C.) output in the case of bipolar timers. It is designed for discharging a capacitor when OUTPUT is in the low state.
8	VCC	Power	Positive Supply: In the case of bipolar timers, the typical supply voltage range falls within 4.5 to 16 volts, with some timers specified to operate up to 18 volts. Most will function with as little as 3 volts. As a recommended practice, decoupling capacitor(s) are commonly used between this pin and GND.

### Modes:

The 555 timer can be employed in various modes for different applications:


1. **Astable Mode (Free-Running):** The 555 acts as an electronic oscillator, suitable for applications like LED flashers, pulse generation, PWM, logic clocks, tone generation, security alarms, and analog-to-digital conversion.
2. **Monostable Mode (One-Shot):** In this mode, the 555 functions as a one-shot pulse generator, useful for timers, bounce-free switches, touch switches, frequency dividers, and more.
3. **Bistable Mode (Latch):** The 555 serves as a set-reset latch, primarily used for switch debouncing.



4. Schmitt Trigger (Inverter) Mode: It functions as a Schmitt trigger inverter gate, helping convert noisy input into a clean digital output.

**Here the IC is used under the Astable mode.**

**Astable mode:**

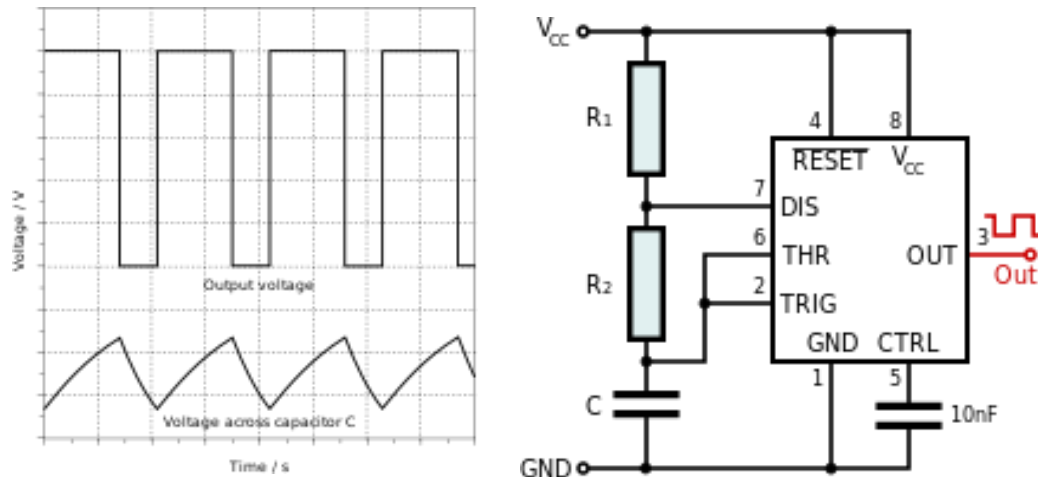

In the astable configuration, the 555 timer generates a continuous stream of rectangular pulses with a specific period. This mode involves two resistors (R<sub>1</sub> and R<sub>2</sub>) and a capacitor (C), with both the threshold and trigger pins connected to the same voltage.

The cycle begins with an uncharged capacitor, and it follows these steps:

1. When the capacitor's voltage is below  $\frac{1}{3} V_{CC}$ , the trigger pin changes the 555's internal latch state, causing OUT to go high and disconnecting the internal discharge transistor.
2. With the discharge pin no longer shorted to ground, the capacitor starts charging through resistors R<sub>1</sub> and R<sub>2</sub>.
3. Once the capacitor charge reaches  $\frac{2}{3} V_{CC}$ , the threshold pin changes the 555's internal latch state again, making OUT go low and saturating the internal discharge transistor.
4. The discharge transistor provides a path for the capacitor to discharge through R<sub>2</sub>.
5. When the capacitor's voltage drops below  $\frac{1}{3} V_{CC}$ , the cycle repeats.

The first pulse involves charging from 0 V to  $\frac{2}{3} V_{CC}$ , while subsequent pulses only charge from  $\frac{1}{3} V_{CC}$  to  $\frac{2}{3} V_{CC}$ . As a result, the first pulse has a longer high time interval than the rest, and the output high interval is longer than the low interval.

The frequency (f) of the pulse is given by:  $f = 1 / [\ln(2) * (R_1 + 2 * R_2) * C]$

The duty cycle (D) is given by:  $D (\%) = [(R_1 + R_2) / (R_1 + 2 * R_2)] * 100$

To create a shorter high time compared to the low time (a duty cycle less than 50%), a fast diode (e.g., 1N4148) can be added in parallel with R2. This diode bypasses R2 during the high part of the cycle.

Voltage-controlled pulse-width modulation is possible by applying a time-varying voltage source to the control pin

### Understanding Duty Cycle:


#### Duty Cycle:

A duty cycle, also known as a power cycle, represents the portion of one complete cycle during which a signal or system is active. It is typically expressed as a percentage or a ratio. The complete cycle, or period, denotes the time required for a signal to go through one on-and-off cycle. The duty cycle (%) can be mathematically expressed as:

$$D = (PW / T) \times 100\%$$

Where:

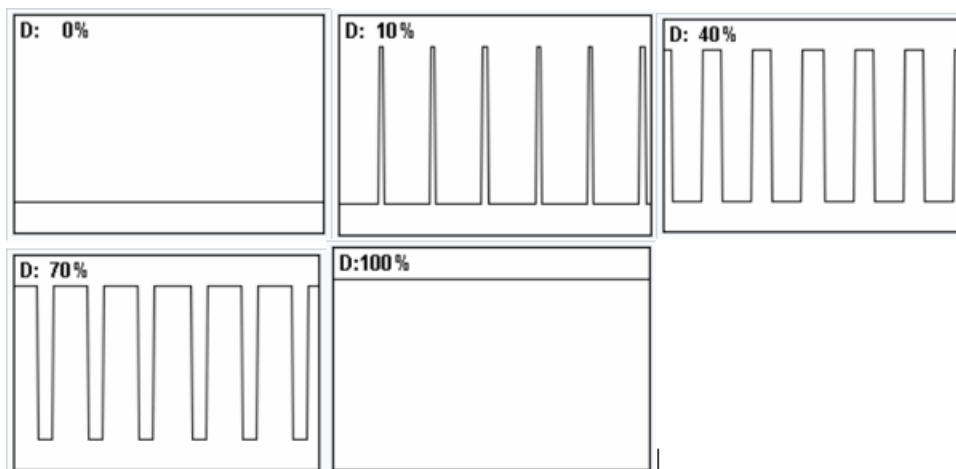- D is the duty cycle
- PW is the pulse width (the active time of the pulse)
- T is the total period of the signal



Consequently, a 60% duty cycle signifies that the signal is active for 60% of the time and inactive for the remaining 40%. The duration of the "on time" for a 60% duty cycle can vary widely, ranging from fractions of a second to days or even weeks, depending on the length of the period.

Duty cycles are commonly used to describe the percentage of time an active signal is present in electrical devices, such as the power switch in a switching power supply, or in living systems, like the firing of action potentials in neurons.

In some publications, the symbol  $\alpha$  is used to represent the duty cycle. Duty cycle, as a ratio, is dimensionless and can be expressed as both a decimal fraction and a percentage.

An alternative term used for duty cycle is duty factor.

#### **Duty Cycle Calculation in our project: ORIGINAL WORK**

##### **IC Charging:**

Capacitor is charging, time constant  $T_C = (R_2 + R_L) * C$

Charge time  $T_{ON} = 0.693 * T_C$

##### **IC Discharging:**

Capacitor is discharging, time constant  $T_D = (R_R) * C$

Discharge time  $T_{OFF} = 0.693 * T_D$

Cycle time =  $T_{ON} + T_{OFF}$

Duty Cycle =  $T_{ON} / (T_{ON} + T_{OFF}) = (R_2 + R_L) / (R_2 + R_L + R_R)$

(assuming  $R_2$  is significantly smaller than potentiometer resistance)

Duty cycle =  $R_L / R_{max}$

( $R_{max}$  is the total possible resistance of potentiometer, unidirectional)

( $R_{max}$  is 50 k Ohm for our potentiometer)

Clearly,

Duty cycle is in linear relationship with potentiometer resistance. Thus, as we increase the potentiometer resistance,  $R_L$ , the duty cycle increases and thus the brightness.

Frequency =  $1/\text{Cycle time} = 1.44 / (R_{max} * C)$

(from the same assumptions.)

This frequency is important, it decides the flickering of the led, the frequency should be high enough to trick the human eye as if it is uniformly glowing.

For reference, normal household LEDs operate at 50 – 60 Hz.

In our circuit, we chose a suitable capacitor,  $C_2 = 100 \text{ nF}$


Frequency =  $1.44 / (50 * 10^3 * 100 * 10^{-9}) = 288 \text{ Hz}$

Suitable.

It shall be noted that we can confirm that the LED flickers by recording it with a camera at high frames per second.

We recorded this at 60 fps and confirmed.

## MOSFET:

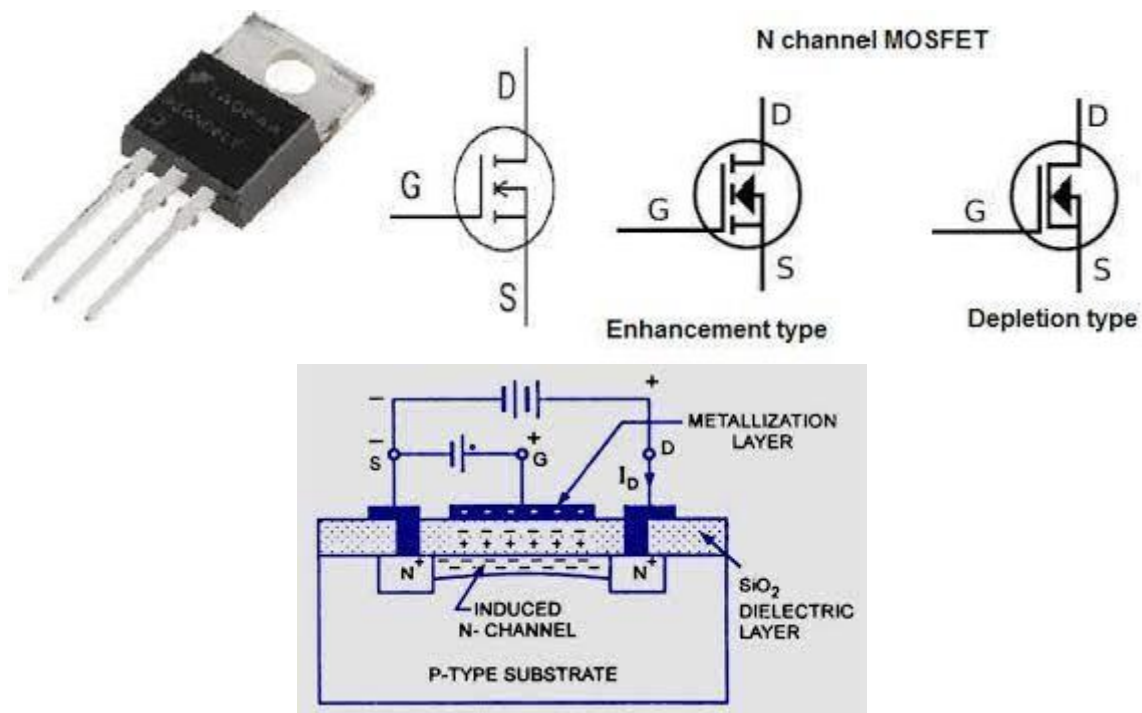

### Basic Understanding and Working of a MOSFET as a Switch for LED Brightness Control:

A Metal-Oxide-Semiconductor Field-Effect Transistor (MOSFET) is a semiconductor device that serves as an efficient and precise electronic switch in our project for LED brightness control. Here is a simplified theory of how a MOSFET operates as a switch in this context:

#### 1. MOSFET Overview:

- A MOSFET is a three-terminal device with a Gate (G), Drain (D), and Source (S).
- It's made up of a semiconductor material and features an insulated gate, which sets it apart from other types of transistors.

#### 2. As a Switch:

- The MOSFET can operate in two modes: as a conducting switch (ON state) and as a non-conducting switch (OFF state).

#### 3. Key Components:

- Gate Terminal (G): The Gate terminal of the MOSFET plays a crucial role. Applying a voltage to the Gate establishes an electric field that controls the flow of current between the Drain and Source.
- Drain Terminal (D): The Drain terminal is where current enters or exits the device.
- Source Terminal (S): The Source terminal is where the current exits or enters the device.

#### 4. Switching Operation:

- OFF State (Non-conducting): When no voltage is applied to the Gate terminal (0V), the MOSFET is in its non-conducting state. This means that current cannot flow from Drain to Source, effectively turning the switch OFF. In our project, this corresponds to the LED being turned off.

- ON State (Conducting): Applying a sufficient positive voltage to the Gate terminal (typically above a threshold voltage) allows current to flow from Drain to Source. The MOSFET is in its conducting state, and the switch is ON. In our project, this corresponds to the LED being turned on.

#### 5. Significance as a Switch in LED Brightness Control:

- In the context of LED brightness control, the MOSFET serves as a crucial switch to control whether the LED is on or off.

- By using a PWM signal from a 555 timer, we can control the MOSFET's Gate voltage to rapidly switch the LED on and off. This generates a Pulse Width Modulated (PWM) signal to regulate the LED's brightness.


- The fast switching action of the MOSFET ensures that the LED responds almost instantaneously to changes in the PWM signal, providing smooth and flicker-free dimming.

#### 6. Energy Efficiency:

- When the MOSFET is in the OFF state, it effectively disconnects the LED from the power supply, minimizing power consumption and enhancing energy efficiency.

The MOSFET's role as a precise and rapid electronic switch is instrumental in achieving dynamic control over LED brightness in our project. By controlling the MOSFET's Gate voltage through a PWM signal, we can smoothly modulate the LED's intensity, making it a vital component in LED brightness control applications.

#### Potentiometer:

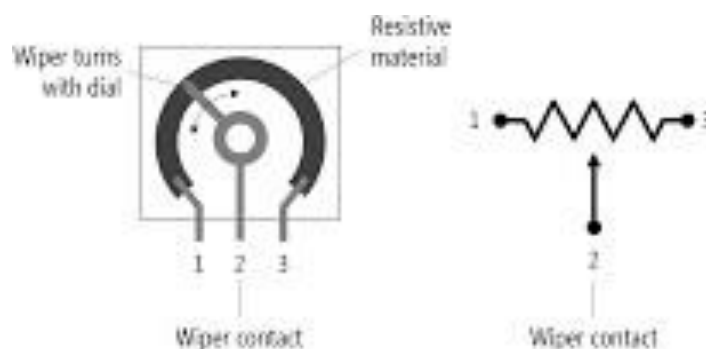

A potentiometer, often referred to as a "pot," is a three-terminal device used in electronics, and in the context of our project for LED brightness control, it plays a crucial role in adjusting the LED's intensity. Here is a simplified explanation of a potentiometer's working and significance:

#### 1. Potentiometer Overview:

- A potentiometer is a variable resistor with three terminals: two fixed ends and a wiper.
- It allows you to manually adjust the resistance between the two fixed ends by turning a knob or lever.

#### 2. As a Variable Resistor:

- In our project, the potentiometer is used to vary the resistance in the circuit.
- By adjusting the knob, the wiper's position along the resistor changes, altering the overall resistance in the circuit.

#### 3. Key Components:

- Fixed End Terminals: These are the two ends of the potentiometer, and they have a fixed resistance value.
- Wiper Terminal: The wiper is a movable contact that can be positioned anywhere between the fixed ends. Its position determines the effective resistance in the circuit.

#### 4. Resistance Adjustment:

- When the wiper is moved towards one of the fixed ends, it decreases the resistance between the wiper and that end. Conversely, moving it toward the other end increases the resistance.

#### 5. Significance in LED Brightness Control:


- The potentiometer is used to set the reference voltage at the Control pin of the 555 timer in our project.
- By changing the resistance using the potentiometer, we can vary the reference voltage, which, in turn, controls the timing of the 555 timer and the LED's brightness.
- It provides a convenient and user-friendly way to adjust the LED's intensity by simply turning a knob.
- The potentiometer's ability to fine-tune the reference voltage is essential for achieving precise and customized LED brightness control.

#### 6. Energy Efficiency:

- By using a potentiometer, we can dynamically change the LED's brightness without significantly affecting energy consumption, making it an energy-efficient method of control.

The potentiometer's role in our LED brightness control project is to serve as a versatile tool for adjusting the reference voltage of the 555 timer, allowing us to finely tune the LED's intensity to suit various lighting requirements.

## LED:

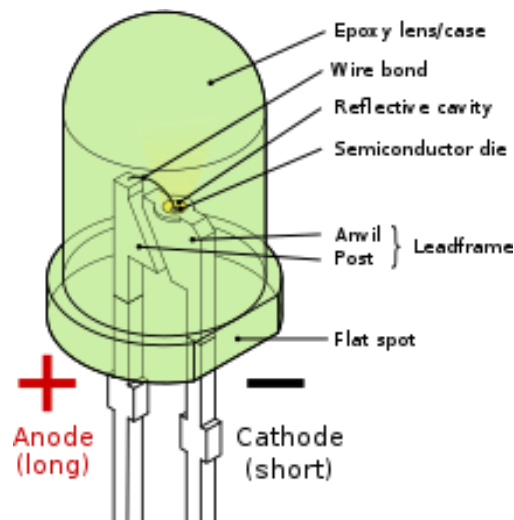

LED (Light Emitting Diode) in LED Brightness Control:

### 1. LED Overview:

- An LED is a semiconductor device that emits light when an electric current passes through it.
- In our project for LED brightness control, the LED is the light source that we aim to control and adjust in terms of its brightness.

### 2. Emission of Light:

- When current flows through the LED, it emits light due to the recombination of electrons and holes within its semiconductor material.
- The color and intensity of the light emitted by the LED depend on its semiconductor material and design.

### 3. Significance in LED Brightness Control:

- The LED is the core component in our project for brightness control, as it is the source of illumination.
- By regulating the current that passes through the LED, we can control its brightness effectively.
- This control is essential for various applications, allowing us to create the desired lighting atmosphere and conserve energy when full brightness is not required.


### 4. Dynamic Control:

- In our project, we use a potentiometer to set the reference voltage and a MOSFET to control the LED's current.
- By modulating the LED's current using a PWM signal from the 555 timer through the MOSFET, we can achieve dynamic brightness control, enabling smooth dimming and adjustments.
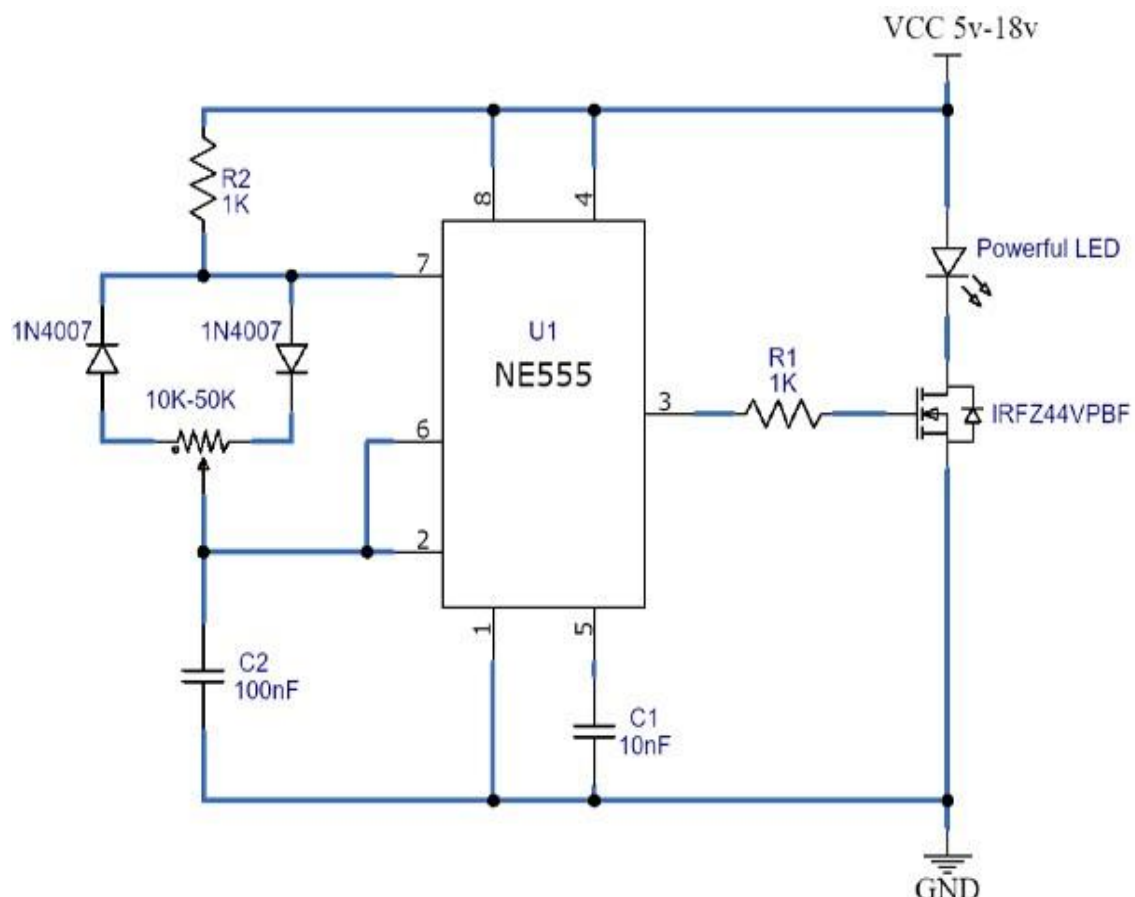
#### 5. Energy Efficiency:

- LED technology is known for its energy efficiency, as it requires significantly less power compared to traditional incandescent lighting.
- LED brightness control not only allows customization but also contributes to energy conservation, making it a sustainable lighting solution.

The LED's role in our project is fundamental, as it is the source of light that we aim to control. By regulating the current passing through the LED, we can achieve precise and dynamic brightness adjustments, catering to various lighting needs while ensuring energy efficiency.





**WORKING EXPLANATION:**

555 timer works as an astable multivibrator and generates PWM pulses.

Circuit includes the timing components like resistors, capacitors and potentiometer.

The potentiometer is there to adjust the duty cycle of the PWM signal.

The higher the duty cycle the greater will be the light intensity, the light intensity will be lower when the duty cycle would be lower.

At the trigger pin, the diodes are used to bypass the cycle of a wired potentiometer during the charging of IC in an astable mode and also to manage the constant frequency irrespective of the duty cycle.

At the end of an IC, MOSFET is connected to run the powerful LED.

**Explanation:**

In the context of an LED dimming circuit, the trigger pin is often used in conjunction with diodes to control the charging cycle of the 555 timer IC operating in astable mode. This configuration helps manage the constant frequency of the circuit while allowing for changes in the duty cycle, which is essential for LED dimming.

Explanation of how this works:

1. **Astable Mode of the 555 Timer:** In astable mode, the 555 timer generates a continuous square wave output, which includes both high and low states. This mode is commonly used for generating pulses or oscillations.

2. **Role of Trigger Pin:** In this mode, the trigger pin (often referred to as the "threshold" pin) is an important element. When the voltage at the trigger pin falls below a certain threshold (determined by the internal reference voltage), it causes the 555 timer's internal circuitry to change state, switching the output from low to high.

3. **Diodes for Bypassing the Potentiometer:** Diodes are introduced to bypass the charging cycle of a wired potentiometer connected to the trigger pin. The wired potentiometer can be thought of as a variable resistor that affects the timing components of the 555 timer, such as the resistor and capacitor values. By bypassing the potentiometer during the charging phase, the timing of the circuit remains consistent and independent of the potentiometer's setting. This ensures that the circuit maintains a constant frequency.

4. **Managing Duty Cycle for LED Dimming:** While the charging cycle remains constant, the potentiometer can be used to control the discharge cycle. The duty cycle of the square wave output, which represents the percentage of time the LED is on during each cycle, can be adjusted by the potentiometer. By controlling the discharge phase, you can effectively dim the LED. When the potentiometer setting results in a longer discharge time, the LED will appear dimmer, and when it's shorter, the LED will appear brighter.

In summary, by using diodes to bypass the potentiometer during the charging phase of the 555 timer in astable mode, the circuit ensures a consistent frequency, while the potentiometer still allows for control over the duty cycle. This setup is commonly used in

LED dimming circuits to achieve variable brightness levels while maintaining a stable frequency of operation.

**The MOSFET serves important purpose here:**

In an LED dimming circuit, especially one designed to drive powerful LEDs, a MOSFET (Metal-Oxide-Semiconductor Field-Effect Transistor) is commonly used to control the LED's brightness. The MOSFET serves as a crucial component in this context for several reasons:

1. **Voltage and Current Handling:** Powerful LEDs often require higher voltage and current levels to operate effectively. MOSFETs are known for their ability to handle high voltage and current levels, making them suitable for driving such LEDs. They act as a reliable switch to control the LED's power supply.
2. **Fast Switching:** MOSFETs can switch on and off rapidly, allowing for precise control of the LED's brightness. This fast switching capability is essential for dimming the LED smoothly without visible flicker or delay.
3. **Efficiency:** MOSFETs are known for their low on-resistance when fully turned on. This means that they introduce minimal voltage drop and power dissipation across the LED driver circuit, making the system more energy-efficient.
4. **PWM (Pulse-Width Modulation) Control:** Most LED dimming circuits use PWM to control the LED's brightness. A MOSFET can be easily modulated using PWM signals generated by the control circuitry. By adjusting the duty cycle of the PWM signal, the MOSFET controls the average current passing through the LED, effectively changing its brightness.
5. **Isolation:** MOSFETs can provide electrical isolation between the control circuitry and the high-power LED, enhancing safety and preventing voltage spikes or noise from affecting the control circuit.
6. **Reliability:** MOSFETs are solid-state devices with no mechanical parts, which means they have a longer lifespan and are less prone to wear and tear compared to mechanical switches.
7. **Small Form Factor:** MOSFETs are available in compact packages, allowing for a compact and space-efficient LED dimming circuit design.

Overall, the MOSFET's ability to handle high power, fast switching, efficiency, and compatibility with PWM control makes it an ideal choice for controlling the brightness of powerful LEDs in dimming circuits. It ensures that the LED can be precisely and smoothly dimmed while maintaining energy efficiency and reliability.

## **PWM (Pulse-Width Modulation) Control:**

What is PWM? Pulse-Width Modulation (PWM) is a technique used to control the brightness of an LED or any other device. It involves rapidly turning the LED on and off at a fixed frequency. By varying the ratio of the time the LED is on (duty cycle) to the time it's off within each cycle, you can effectively control the average power delivered to the LED, and thus its brightness.

**Role of the MOSFET:** In an LED dimming circuit, a MOSFET acts as the switch that controls the LED's power supply based on the PWM signal. Here's how it works:

- **Fast Switching Action:** MOSFETs have an inherent ability to switch very quickly between the "on" and "off" states. When the PWM control signal dictates that the LED should be on, the MOSFET swiftly turns on, allowing current to flow from the power supply to the LED. This action happens almost instantaneously.
- **Precise Control:** The PWM control signal typically has a fixed frequency. The duty cycle, which is the percentage of time the LED is on within each PWM cycle, determines the brightness. For example, a 50% duty cycle means the LED is on for half of the cycle and off for the other half, resulting in moderate brightness.
- **Smooth Dimming:** By changing the duty cycle of the PWM signal, you can smoothly adjust the LED's brightness. For instance, if the duty cycle is increased to 75%, the LED is on for most of the cycle, making it brighter. Reducing the duty cycle to 25% makes the LED dimmer. The MOSFET's fast switching action ensures that these changes in brightness are practically instantaneous and appear continuous to the human eye, resulting in smooth and flicker-free dimming.
- **Energy Efficiency:** When the MOSFET is off (during the "off" part of the PWM cycle), it effectively disconnects the LED from the power supply, minimizing power consumption. This on-and-off switching, along with the low on-resistance of MOSFETs, makes LED dimming very energy-efficient.

In summary, the MOSFET in an LED dimming circuit acts as a rapid switch that turns the LED on and off in sync with the PWM control signal. This enables precise control of the LED's brightness, allowing it to be smoothly and efficiently dimmed without visible flicker or delay. The fast switching action of the MOSFET ensures that the LED responds quickly to changes in the PWM signal, resulting in the desired level of illumination.

**If you did not connect a MOSFET** and used a different method to control LED brightness, such as limiting current or voltage through resistors, here's what would happen:

**Lack of Fast Response (Specific to Point 4):** When not using a MOSFET with PWM control, the dimming process would likely lack the fast response and precision needed for smooth LED dimming. Adjusting brightness through resistors or other methods typically results in a slower response and may introduce noticeable flicker or delays in the LED's brightness.


changes. The LED's illumination would not adapt quickly to changes in the control signal, which can be problematic in applications where rapid and seamless dimming is required. In contrast, a MOSFET's fast switching action in response to PWM signals ensures that the LED's brightness can be adjusted almost instantaneously, providing a smoother and more responsive dimming experience.

If you did not connect a MOSFET in the LED dimming circuit and, instead, relied on a different method to control the LED's brightness, several consequences and limitations would arise:


1. **Limited Dimming Control:** Without a MOSFET, you would likely have to rely on other methods, such as using resistors to control current or voltage to the LED. While this can dim the LED to some extent, it offers limited control and may not provide smooth or precise dimming.
2. **Inefficiency:** Dimming by limiting current or voltage through resistors dissipates excess power as heat. This approach can be highly inefficient, especially when dimming powerful LEDs, as it results in wasted energy.
3. **Lack of Fast Response:** Resistor-based dimming methods lack the fast response and precision that PWM control with a MOSFET offers. LEDs dimmed with resistors may exhibit noticeable flicker or delayed response when brightness is adjusted.
4. **Less Flexibility:** With resistors or other methods, changing the brightness level typically involves manually adjusting components. In contrast, PWM control through a MOSFET allows for dynamic and automated dimming control, making it suitable for applications where real-time adjustments are needed.
5. **Heat Generation:** Inefficient dimming methods can generate heat in the LED driver circuit, potentially requiring additional cooling mechanisms. MOSFET-based dimming minimizes heat generation and is more energy-efficient.

In summary, not using a MOSFET for LED dimming would result in less precise and less efficient control over the LED's brightness. It may limit your ability to achieve smooth and dynamic dimming, which is often desired in applications like lighting control, where rapid adjustments in brightness are necessary. The use of a MOSFET, with its fast switching action and PWM capability, provides a more effective and versatile solution for LED dimming.


## DEMONSTRATION OF PROJECT:

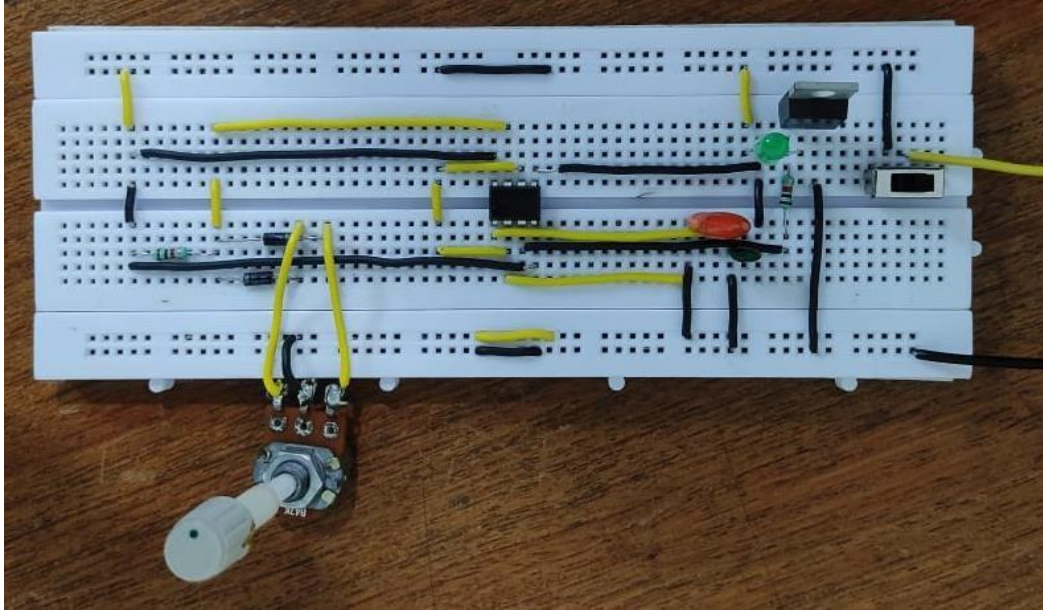


Picture 1 When switched off

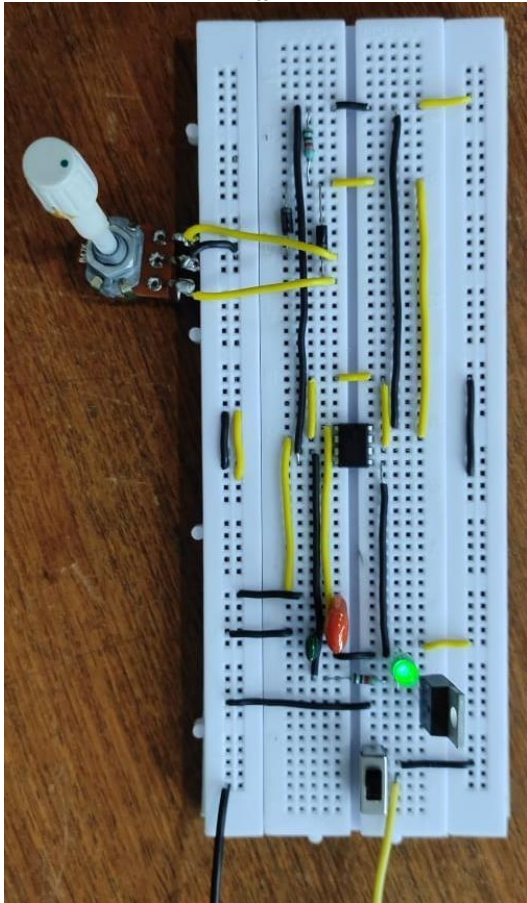

Picture 2 pot at minimum

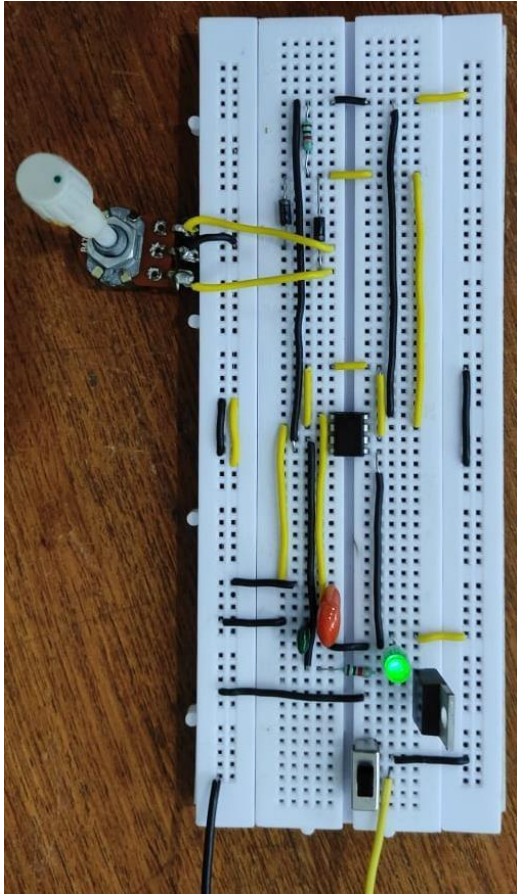


Picture 3 pot at level 1

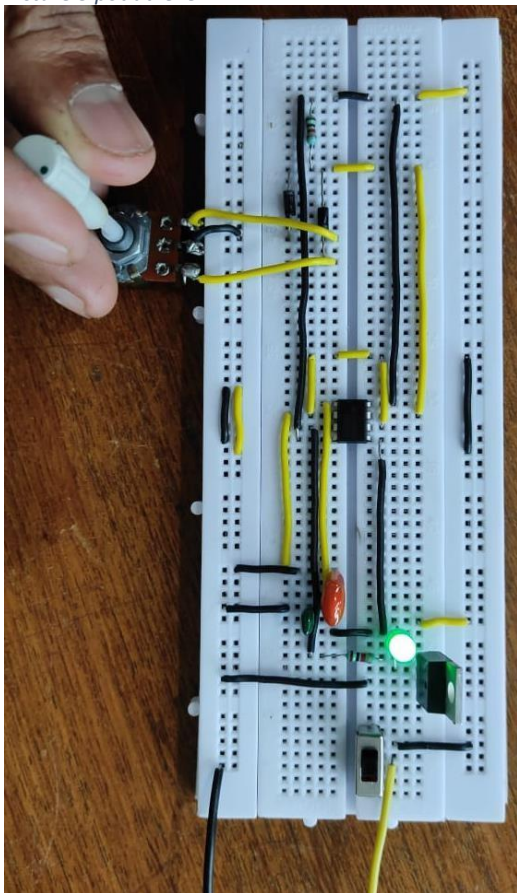


Picture 4 pot at level 2




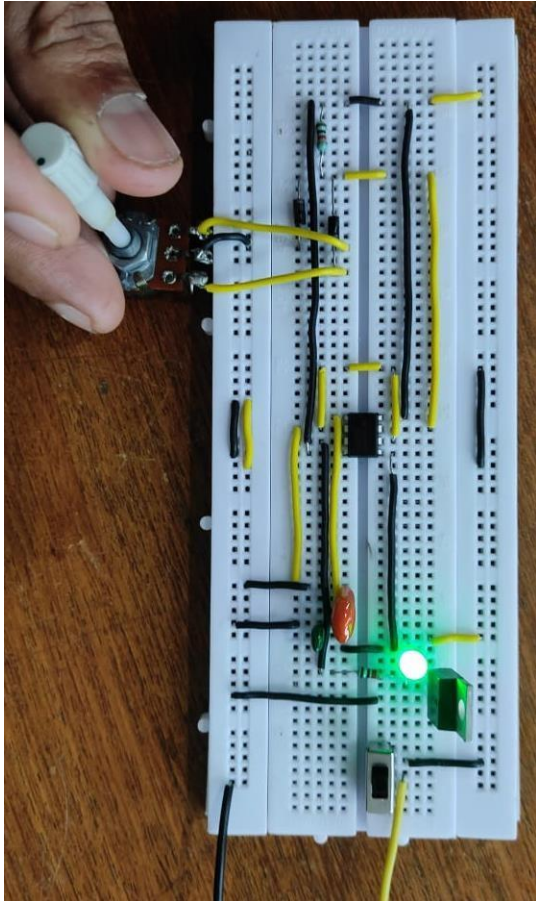


Picture 5 pot at level 3

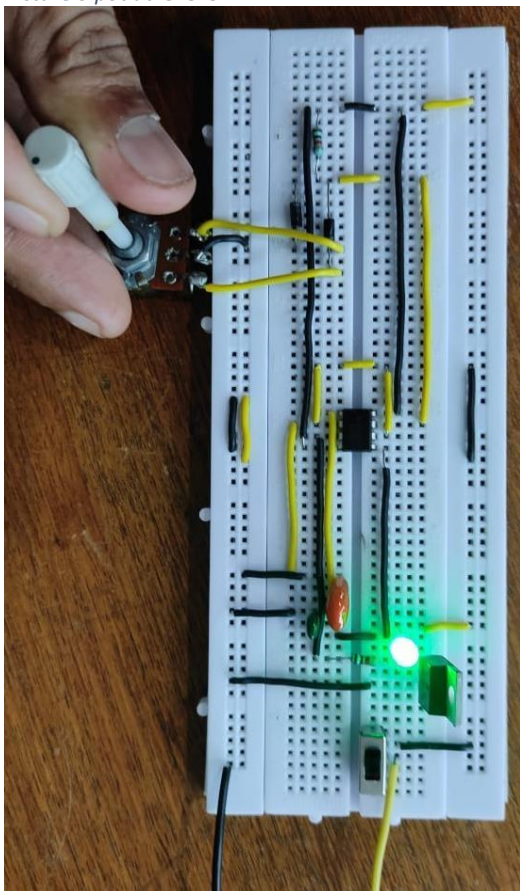

Picture 4 pot at level 2

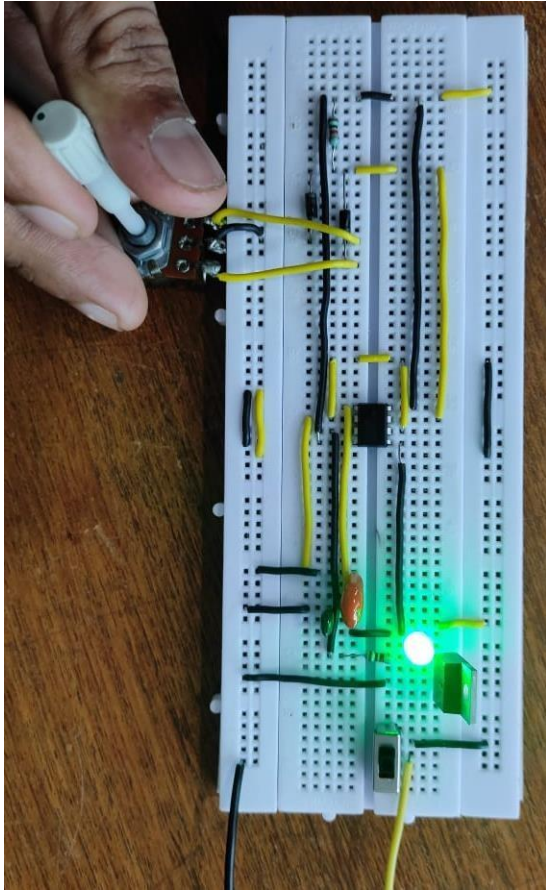

*Picture 7 pot at level 5*

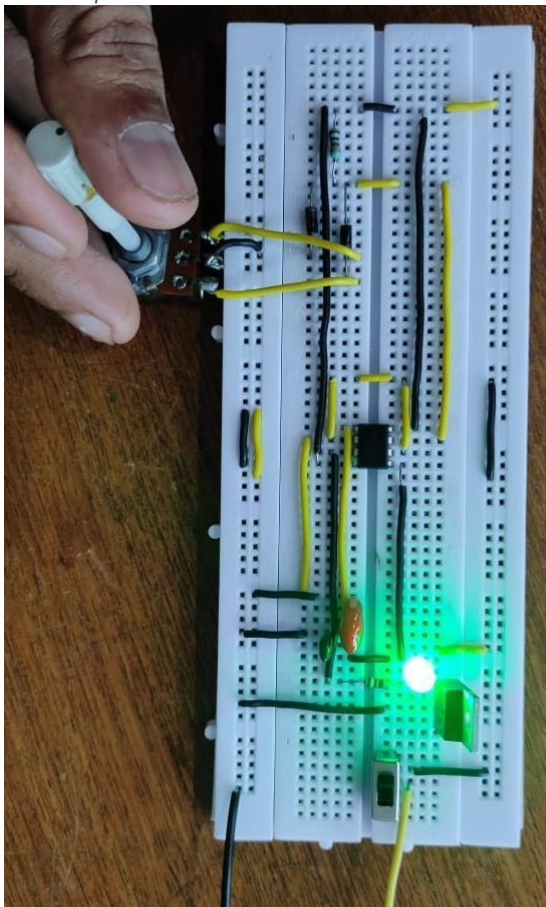

*Picture 8 pot at maximum*



## **What Did We Learn in This Project?**

Throughout this project, we gained valuable insights into several key areas:

1. **Electronic Circuit Design:** We learned how to design a circuit using components like the potentiometer and 555 timer IC to control the brightness of an LED. This included understanding the roles of different components and how they interact.
2. **Component Interactions:** We discovered how the potentiometer and 555 timer IC work together to regulate the LED's intensity. This deepened our knowledge of how various components can collaborate in electronic systems.
3. **New component learning:** Used a 555 timer and MOSFET for the first time with proper understanding and got to apply potentiometer in circuit with a relatively complex circuitry.
4. **Practical Application:** We applied theoretical knowledge to practical work. This project reinforced our understanding of how circuits function in real-world situations.
5. **Problem-Solving:** We encountered challenges along the way and had to think creatively to overcome them. This helped us enhance our problem-solving skills.

## **Difficulties Faced and How We Overcame Them:**

1. **Circuit Stability:** Initially, we faced issues with the circuit's stability. The 555 timer IC was not producing consistent results. To overcome this, we carefully reviewed the connections, ensuring they were correct and secure.
2. **Potentiometer Calibration:** Calibrating the potentiometer for precise brightness control was a bit tricky. We solved this by adjusting the potentiometer and the resistor values until we achieved the desired control range.
3. **Understanding the 555 Timer:** Understanding the internal workings of the 555 timer IC required some research. We read documentation and online resources to gain a better grasp of its functionality.
4. **Overheating and component failure:** Quite a few times, components like LED and MOSFET burned. We identified that this happens when we exceed the rated voltage and hence decided to use lower power and a switch a safety check before power input.

By facing and overcoming these difficulties, we not only completed the project successfully but also developed practical skills and knowledge that will be valuable in future endeavours.

## **CONCLUSION:**

### **Project summary:**

In this project, we designed a circuit to control LED brightness using a potentiometer and a 555 timer IC. We successfully learned how to create an adjustable lighting system, enhancing our knowledge in electronic circuit design, component interaction, and practical application.

### **What we learned:**

Electronic circuit design principles.

How a potentiometer and 555 timer IC collaborate to control LED brightness.

Problem Solving skills in circuit stability and calibration.

### **Future Enhancements:**

To expand this project, we could explore additional features like remote control, more complex lighting patterns, or integration with smart systems for enhanced automation and user-friendliness.

### **References:**

Wikipedia: 555 timer IC:

[https://en.wikipedia.org/wiki/555\\_timer\\_IC#:~:text=A%20555%20timer%20can%20be,into%20a%20clean%20digital%20output.&text=%2C%20which%20causes%20the%20signal%20to,input%20pins%20of%20the%20timer.](https://en.wikipedia.org/wiki/555_timer_IC#:~:text=A%20555%20timer%20can%20be,into%20a%20clean%20digital%20output.&text=%2C%20which%20causes%20the%20signal%20to,input%20pins%20of%20the%20timer.)

Circuits-diy: LED dimmer circuit:

<https://www.circuits-diy.com/led-dimmer-circuit-with-555-timer/>

Wikipedia and some Googled data: Duty Cycle, Astable mode, LED, MOSFET, Potentiometer, etc.

### **Software used:**

MS Word to type the report

Circuit-diagram.org to design the circuit

**We sincerely thank the ELP101 team, professors, instructors, and Teaching Assistants for their valuable support and leaning.**

**ELP101 was a fabulous course and we are thankful to complete it.**